


# Le dipôle RL

10) a) Loi des mailles

$$u_1 + u_2 - E = 0$$

$$u_1 + r i + L \frac{di}{dt} = E$$
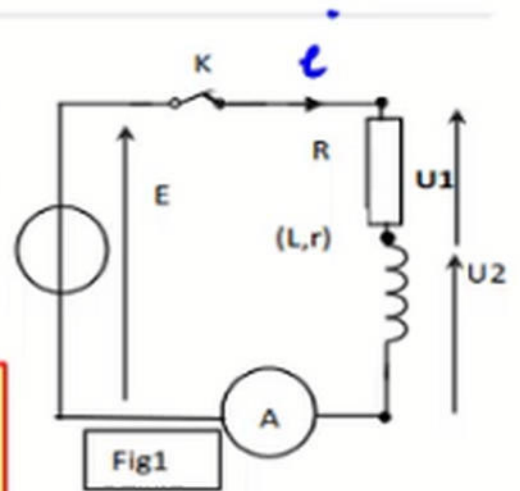
$$u_1 = u_R = R i \Rightarrow i = \frac{u_1}{R}$$



$$\Rightarrow u_1 + r \frac{u_1}{R} + L \frac{d}{dt} \left( \frac{u_1}{R} \right) = E$$

$$u_1 \left( 1 + \frac{r}{R} \right) + \frac{L}{R} \frac{d}{dt} u_1 = E$$

$$u_1 \left( \frac{R+r}{R} \right) + \frac{L}{R} \frac{d}{dt} u_1 = E$$

$$(R+r) u_1 + L \frac{d u_1}{dt} = R E$$

$$\frac{d u_1}{dt} + \frac{R+r}{L} u_1 = \frac{R E}{L} ; \frac{R+r}{L} = \frac{1}{\tau}$$

$$\Rightarrow \frac{d u_1}{dt} + \frac{1}{\tau} u_1 = \frac{R E}{L}$$

$$b) u_1(t) = A e^{-kt} + B$$

$$* \text{ at } t=0 \quad i^0 = 0 \Rightarrow u_1 = R i^0 = 0$$

$$\Rightarrow 0 = A e^0 + B \Rightarrow \boxed{A = -B}$$

$$* \frac{du_1}{dt} = -kA e^{-kt} + 0$$

$$* \text{ eq. diff} \Rightarrow -kA e^{-kt} + \frac{1}{\sigma} (A e^{-kt} + B) = \frac{ER}{L}$$

$$\Rightarrow -kA e^{-kt} + \frac{B}{\sigma} + \frac{A}{\sigma} e^{-kt} = \frac{ER}{L}$$

$$\Rightarrow \underbrace{A e^{-kt}}_{\text{Vanis}} \left( \underbrace{\frac{1}{\sigma} - k}_{ct} \right) + \underbrace{\frac{B}{\sigma}}_{ct} = \underbrace{\frac{ER}{L}}_{ct}$$

$$\Rightarrow \frac{1}{\sigma} - k = 0 \quad \text{el.} \quad \frac{B}{\sigma} = \frac{ER}{L}$$

$$\boxed{k = \frac{1}{\sigma}} \quad \text{el.} \quad B = \frac{\sigma ER}{L} = \frac{\sqrt{E+R}}{(R+L)\sqrt{}}$$

$$\Rightarrow K = + \frac{1}{s} \quad B = \frac{RE}{R+s} \quad \text{et}$$

$$A = -B = - \frac{RE}{R+s}$$

$$\Rightarrow u_1 = - \frac{RE}{R+s} e^{-\frac{t}{s}} + \frac{RE}{R+s}$$

$$u_1(t) = \frac{RE}{R+s} \left( 1 - e^{-\frac{t}{s}} \right)$$

$$c) u_A(t) = u_B(t) = E - u_1$$

$$u_2(t) = E - \frac{RE}{R+s} \left( 1 - e^{-\frac{t}{s}} \right)$$

$$= E - \frac{RE}{R+s} + \frac{RE}{R+s} e^{-\frac{t}{s}}$$

$$= \frac{\cancel{RE} - \cancel{RE} + RE}{R+s} + \frac{RE}{R+s} e^{-\frac{t}{s}}$$

$$\Rightarrow u_2(t) = \frac{R E}{R+v} e^{-\frac{t}{\tau}} + v \frac{E}{R+v}$$

AVec  $U_0 = \frac{R E}{R+v}$  et  $b = \frac{v E}{R+v}$

Rq:  $I_L = \frac{E}{R+v}$

2g e)

\* b)


$$t=0 \quad i=0 \Rightarrow$$

$$u_1 = R i = 0$$

$\Rightarrow$  comme (1)

$$* t=0 \quad u_2 = \frac{R E}{R+v} + \frac{v E}{R+v} = \frac{(R+v) E}{R+v} = E$$

$\Rightarrow$  comme (2)

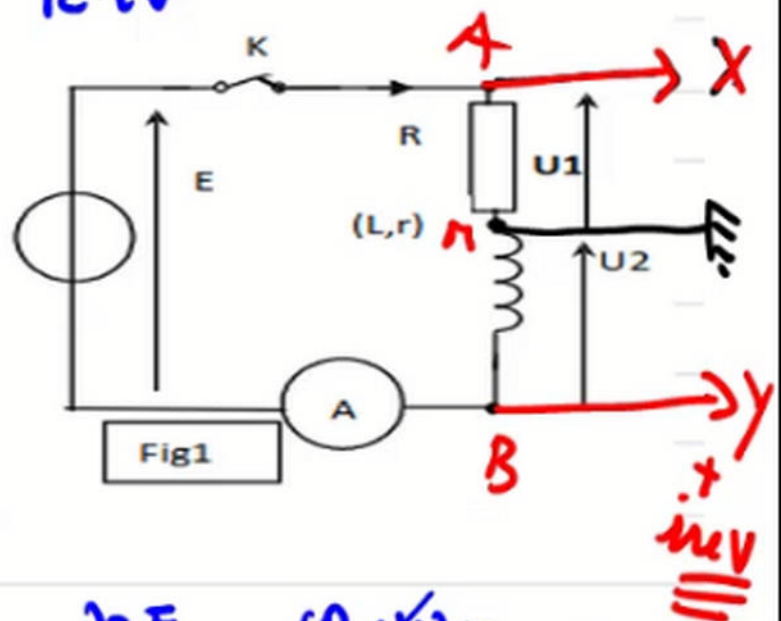

$$c) * \text{ at } t = 0 \quad u_2 = E$$

$$\Rightarrow E = 6 \text{ V}$$

$$* U_0 = R \frac{E}{R+r} = R I_0$$
$$= (U_1)_{\max} = 5 \text{ V}$$

$$3^{\circ}) a) I_p = \frac{U_0}{R}$$

$$I_p = \frac{5}{50} = 0,1 \text{ A}$$

b) Regime permanent

$$\Rightarrow E = (R+r) I_p \quad (1)$$

$$U_0 = R I_p \quad (2)$$

$$\frac{v}{\lambda} = \frac{E}{u_0} = \frac{R+v}{R}$$

$$\Rightarrow R+v = R \frac{E}{u_0}$$

$$v = \frac{RE}{u_0} - R$$

$$\Rightarrow v = R \left( \frac{E}{u_0} - 1 \right)$$

AN  $v = 50 \left( \frac{6}{5} - 1 \right) = 10 \Omega$ .

c) méthode de la tangente  
à l'origine  $\Rightarrow \delta = 2 \text{ ms}$

$$\delta = t_A$$

$$\mathcal{E} = \frac{L}{R + r}$$

$$L = (R + r) \mathcal{E}$$

$$L = (50 + 10) \cdot 2 \cdot 10^{-3}$$

$$L = 0,12 \text{ H}$$