

## Chapitre : LE DIPOLE RL


Corrigé Exercice 4:

1. Loi des mailles :

$$u_{BC} + u_{AB} - \mathcal{E} = 0$$

$$Ri + ri + L \frac{di}{dt} = \mathcal{E}$$
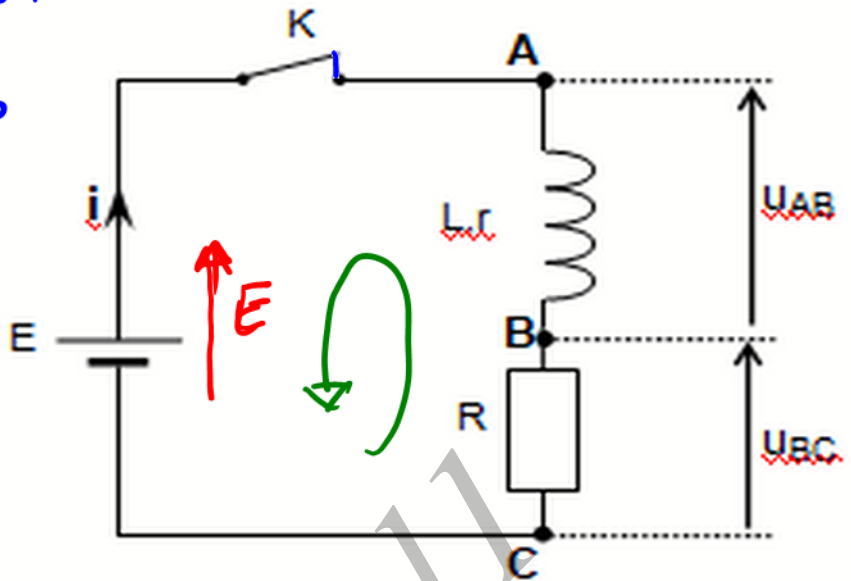
$$(R+r)i + L \frac{di}{dt} = \mathcal{E}$$



$$i + \frac{L}{R+r} \frac{di}{dt} = \frac{\mathcal{E}}{R+r}$$

2. a.  $i(t) = A e^{-\alpha t} + B$

$$\frac{di}{dt} = -\alpha A e^{-\alpha t}$$

① donne:  $A e^{-\alpha t} + B - \alpha A \frac{L}{R+r} e^{-\alpha t} = \frac{\mathcal{E}}{R+r}$

$$A e^{-\alpha t} \left[ 1 - \alpha \frac{L}{R+r} \right] + B = \frac{\mathcal{E}}{R+r}$$

Ceci est vrai  $\forall t$  si

$$B = \frac{\mathcal{E}}{R+r}$$

## Chapitre : LE DIPOLE RL

$$1 - \lambda \frac{L}{R+r} = 0 \Leftrightarrow \lambda = \frac{1}{\frac{L}{R+r}} = \frac{1}{\tau}$$

$$a \quad t=0 \quad i' = A + B = 0 \Leftrightarrow A = -B = -\frac{\bar{E}}{R+r}$$

$$b. \quad i = \frac{\bar{E}}{R+r} (1 - e^{-t/\tau})$$

$$* \quad u_{BC} = R i = \frac{R \bar{E}}{R+r} (1 - e^{-t/\tau})$$

$$* \quad u_{AB} = \bar{E} - u_{BC} = \bar{E} - \frac{R \bar{E}}{R+r} (1 - e^{-t/\tau})$$

$$u_{AB} = \bar{E} - \frac{R \bar{E}}{R+r} + \frac{R \bar{E}}{R+r} e^{-t/\tau}$$

$$u_{AB} = \frac{r \bar{E}}{R+r} + \frac{R \bar{E}}{R+r} e^{-t/\tau}$$

3.

a. En régime permanent

$$i = I = \frac{\bar{E}}{R+r}$$

b.

$$u_{BC} = \frac{R \bar{E}}{R+r} = R I$$

$$u_{AB} = \frac{r \bar{E}}{R+r} = r I$$

4 a. En régime permanent :

$$U_{BC} = R I \Leftrightarrow I = \frac{U_{BC}}{R}$$

$$\text{AN } I = \frac{7}{35} = 0,2 \text{ A}$$

$$* U_{AB} = r I \Leftrightarrow r = \frac{U_{AB}}{I} = \frac{2}{0,2} = 10 \Omega$$

$$I = \frac{E}{R+r} \Leftrightarrow E = (R+r) I$$

$$\text{AN } E = (35 + 10) \times 0,2 = 9 \text{ V.}$$

$$\text{Dq : } E = U_{AB} + U_{BC} = 9 \text{ V}$$

b.


$$At = \tau$$

$$U_{BC} = 0,63 R I$$

$$U_{BC} = 0,63 \times 7$$

$$U_{BC} = 4,41 \text{ V}$$

$$\Rightarrow \tau = 2 \text{ ms}$$

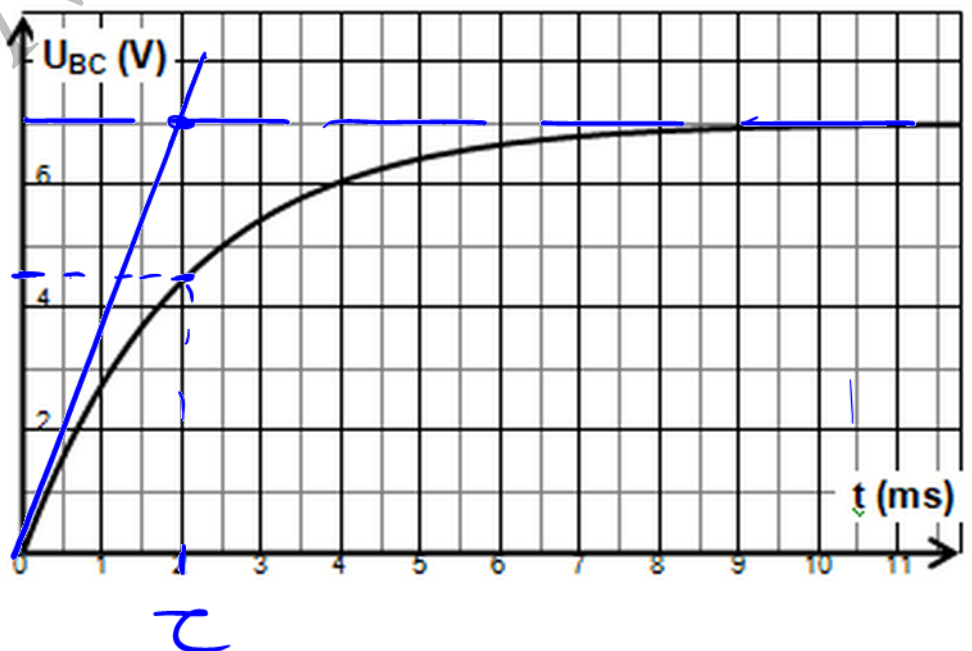

$$\tau = \frac{L}{R+r} \Rightarrow L = \tau (R+r)$$

$$L = 2 \cdot 10^{-3} (35 + 10) = 9 \cdot 10^{-2} \text{ H}$$

**Rq :** 
$$u_{AB} = E - \frac{R\bar{E}}{R+r} (1 - e^{-t/\tau})$$

à  $t = \tau \Rightarrow u_{AB} = E + \frac{R\bar{E}}{R+r} \times 0,63 = 0,37E$

$$u_{AB} = 9 - 4,47 = 4,53 \text{ V.}$$

$$\Rightarrow \tau = 2 \text{ ms.}$$