

LE DIPOLE RC

II 1. Loi des mailles:

$$u_{BD} + u_{AB} = 0$$

$$Ri + u_{AB} = 0$$

$$\text{or } i = \frac{dq}{dt} = C \cdot \frac{du_{AB}}{dt}$$

$$RC \frac{du_{AB}}{dt} + u_{AB} = 0 \quad (2)$$

2. $u_{AB} = E e^{-\alpha t}$

$$\frac{dE}{dt} = E(-\alpha e^{-\alpha t}) = -\alpha E e^{-\alpha t}$$

$$-RC\alpha E e^{-\alpha t} + E e^{-\alpha t} = 0$$

$$E e^{-\alpha t} (1 - RC\alpha) = 0$$

$$1 - RC\alpha = 0 \Rightarrow \alpha = \frac{1}{RC} = \frac{1}{\tau}$$

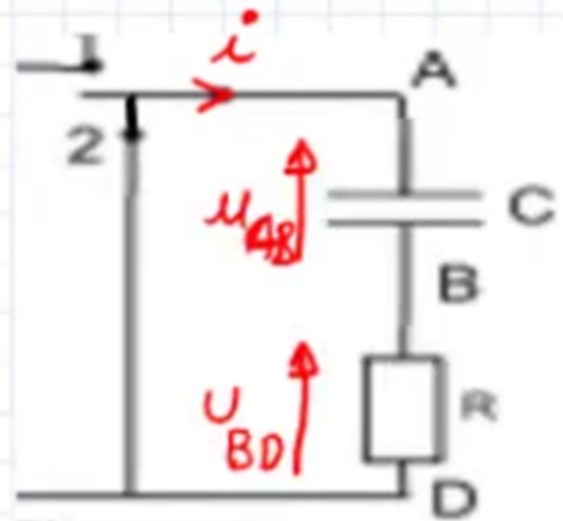


Figure 1

LE DIPOLE RC

3 a. $u_{BD} = -u_{AB}$

A $t=0 \Rightarrow u_{AB} = E \Rightarrow u_{BD} = -E = -5$

b. $u_{BD}(t) = -u_{AB}(t)$

$$u_{BD}(t) = -E e^{-t/\tau}$$

4. Lorsque $t \rightarrow \infty \Rightarrow u_{BD} \rightarrow 0$.



$$E_e = \frac{1}{2} C \cdot u_c^2 = \frac{1}{2} C E^2$$

$$E_e = \frac{1}{2} 100 \cdot 10^{-9} \times 5^2 = 1,25 \cdot 10^{-6} \text{ J.}$$