
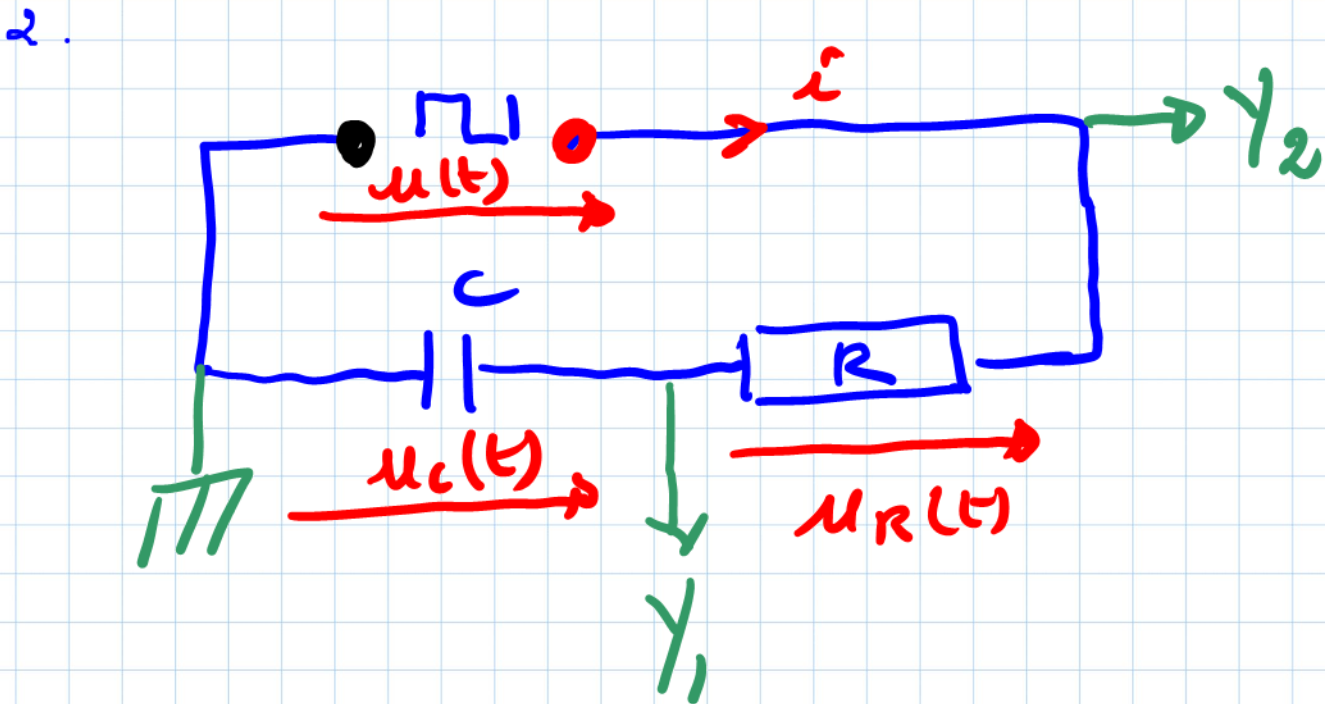


LE DIPOLE RC

Corrigé exercice 5 :

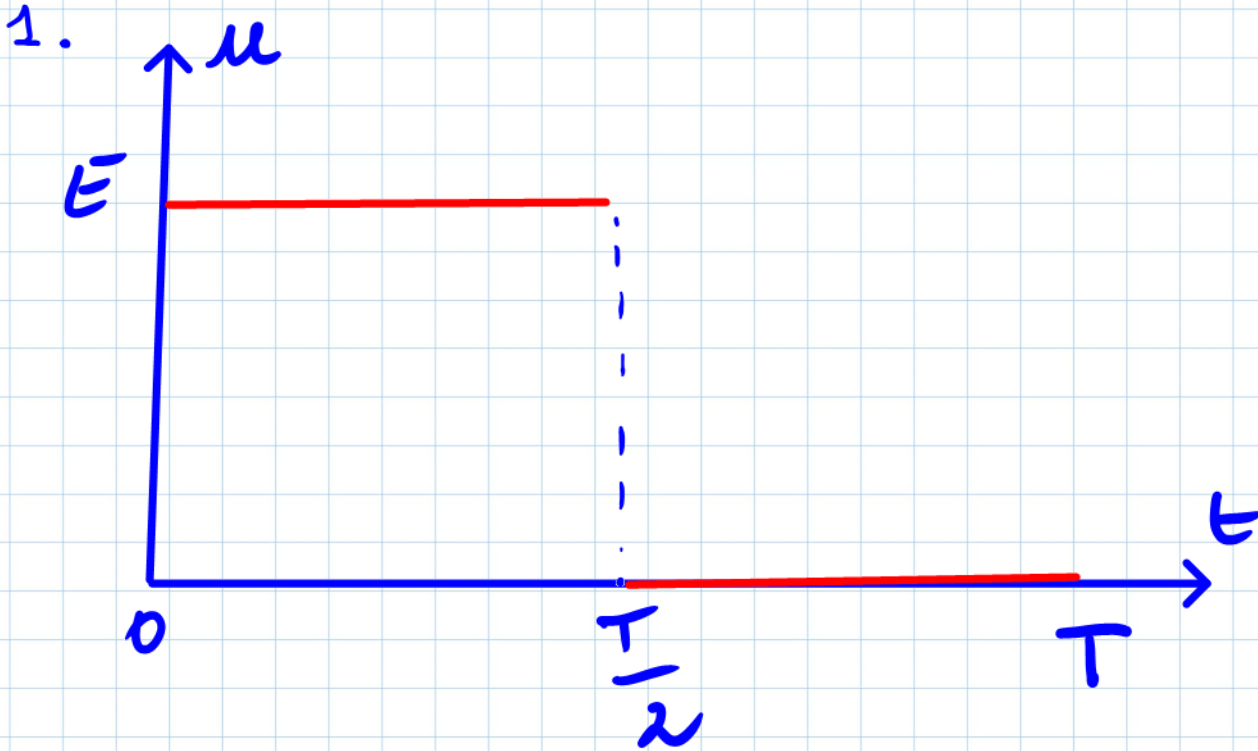

LE DIPOLE RC

b. Loi des mailles :

$$u_c + u_R - u(t) = 0.$$

$$t \in [0, T/2] \quad u(t) = E$$

$$u_c + R i = E$$

$$\text{or } \left. \begin{array}{l} i = \frac{dq}{dt} \\ q = C \cdot u_c \end{array} \right\} i = C \cdot \frac{du_c}{dt}$$

$$u_c + RC \frac{du_c}{dt} = E$$

①

LE DIPOLE RC

$$c) \quad u_c(t) = A(1 - e^{-\alpha t}) = A - A e^{-\alpha t}$$

$$c_1. \quad \frac{du_c}{dt} = \frac{d}{dt} [A - A e^{-\alpha t}]$$

$$= \alpha A e^{-\alpha t}$$

① donne.

$$A(1 - e^{-\alpha t}) + RC \alpha A e^{-\alpha t} = E$$

$$A - A e^{-\alpha t} + RC \alpha A e^{-\alpha t} = E$$

$$A e^{-\alpha t} [-1 + RC \alpha] + A = E$$

Ceci est vrai $\forall t$ si :

$$\begin{cases} -1 + RC \alpha = 0 \\ A = E \end{cases} \Rightarrow \begin{cases} \alpha = \frac{1}{RC} \\ A = E \end{cases}$$

LE DIPOLE RC

$$A = E = 10 \text{ V}$$

$$\alpha = \frac{1}{RC} = \frac{1}{10^3 \times 10^{-6}} = 10^3 \text{ s}^{-1}$$

c₂. physiquement $A = E : U_{\text{max}}$

$$\alpha = \frac{1}{RC} = \frac{1}{\tau} : \text{inverse de la constante de temps}$$

$$d. * T_2 = 2RC = 2\tau.$$

$$u_c(t) = E(1 - e^{-t/\tau})$$


$$t \in [0, T_2].$$

$$\text{si } t=0 \Rightarrow u_c = E(1 - e^{-\frac{0}{\tau}}) = 0.$$

$$\begin{aligned} \text{si } t = \frac{T_2}{2} &\Rightarrow u_c = E(1 - e^{-\frac{T_2}{2\tau}}) \\ &= E(1 - e^{-\frac{2\tau}{2\tau}}) \end{aligned}$$

LE DIPOLE RC

$$u_c = E(1 - e^{-t}) = 0,86E = 8,6V$$

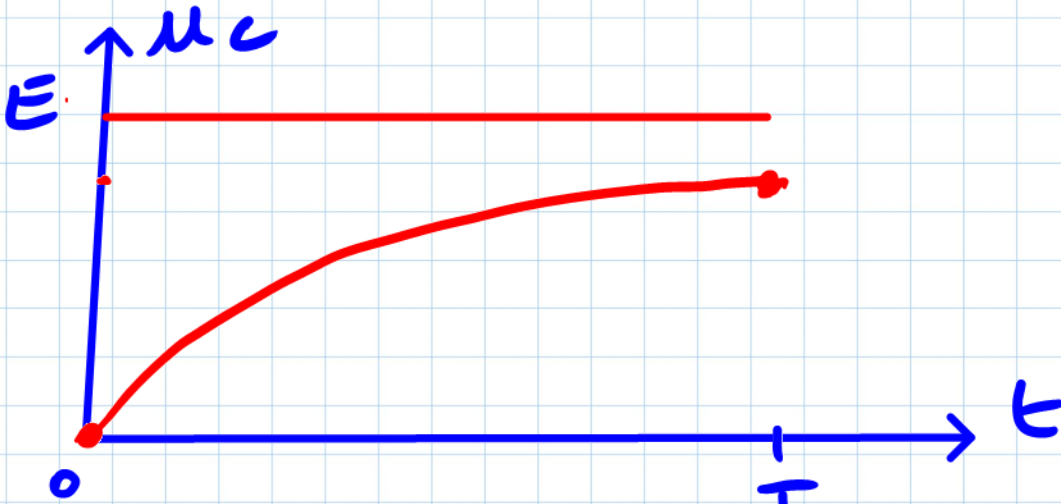

le condensateur n'est pas totalement chargé à $t = T/2$.

LE DIPOLE RC

$$* \quad \frac{T}{2} = 8RC$$


$$u_c = E(1 - e^{-t/\tau})$$

$$\text{à } t=0 \quad u_c = E(1 - e^0) = 0$$

$$\text{à } t = \frac{T}{2} = 8RC = 8\tau$$

$$u_c = E(1 - e^{-\frac{8\tau}{\tau}})$$

$$= E(1 - e^{-8}) = E$$

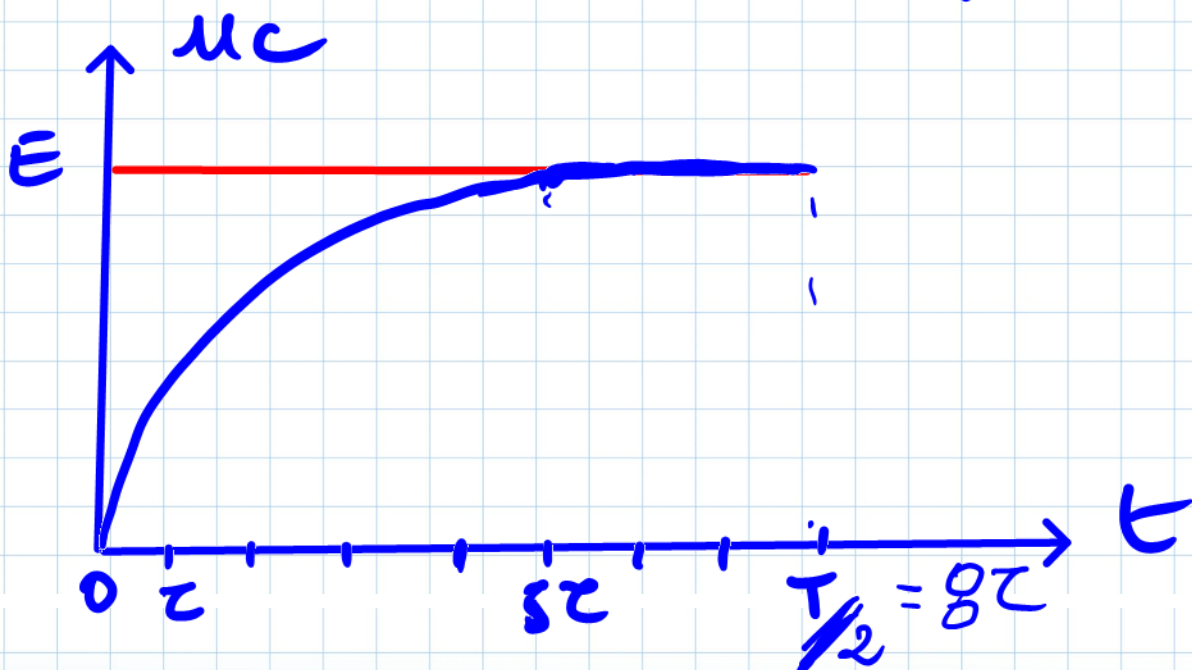

LE DIPOLE RC

e) le condensateur est totalement chargé si $\frac{T}{2} \geq 5\tau$.

$$T \geq 10\tau$$

$$N = \frac{1}{f}$$

$$N \leq \frac{1}{10\tau} = N_{\max}$$

$$\alpha = \frac{1}{\tau} = 10^3 \text{ s}^{-1} \Rightarrow \tau = 10^{-3} \text{ s}$$

$$N_{\max} = \frac{1}{10 \times 10^{-3}} = 100 \text{ Hz}$$

$$N \leq 100 \text{ Hz} = N_{\max}$$

LE DIPOLE RC

$$f) \quad E_e = \frac{1}{2} C \cdot U_c^2$$

lorsque le condensateur est totalement chargé $U_c = E$

$$E_e = \frac{1}{2} C \cdot E^2$$

$$E_e = \frac{1}{2} 10^{-6} \times 10^2 = 5 \cdot 10^{-5} \text{ J}$$

$$g) \quad q(t) = C \cdot u_c(t)$$

$$q_{\max} = C \cdot E$$

$$q = 0,99 q_{\max}$$

$$C \cdot u_c = 0,99 C \cdot E$$

$$C \cdot E (1 - e^{-t/\tau}) = 0,99 C E$$

LE DIPOLE RC

$$1 - e^{-t/\tau} = 0,99 \Leftrightarrow e^{-t/\tau} = 0,01.$$

Rq: $\ln e^x = x.$

$$\Rightarrow \ln e^{-t/\tau} = \ln 0,01$$

$$-\frac{t}{\tau} = -4,6 \Rightarrow t = 4,6\tau = 4,6 \cdot 10^{-3} \text{ s}$$

* $q = 0,999 q_{\max} \Leftrightarrow c \cdot u_c = 0,999 c E$

$$\cancel{c} (1 - e^{-t/\tau}) = 0,999 \cancel{c} E$$

$$1 - e^{-t/\tau} = 0,999 \Rightarrow e^{-t/\tau} = 0,001$$

$$\ln(e^{-t/\tau}) = \ln(0,001) = -6,9$$

$$-t/\tau = -6,9 \Leftrightarrow t = 6,9\tau = 6,9 \cdot 10^{-3} \text{ s}$$